

Kyle Loyka
Homework 1
ECEN 449-503
Due: 10 February 2016

```

//Kyle Loyka
//ECEN 449 - 503
//Homework 1
//Question 1

`timescale 1ns/1ps /* added tilde (`) */

module BuggyCode(input A, input B, input clock, output C);
    wire flag;

    //reg [7:0] data = 8'b10101011;
    //not needed. changed value to correct bit length identifier.

    reg D; /* changed to reg */
    assign flag = A & B; /* added 'assign' statement */
    And and1(A,B,C); /* module needs name. */
    always @(posedge clock) /* took out the semi-colon */
        begin
            if (flag == 0)
                begin
                    D <= A + C; /* took out assign, so D only
                                changes when the desired
                                conditions are met */

                    //data <= data & 8'b11111111;
                    /* removed. Not needed. why is this even
                    here? The 'data' value will never change */

                end /* put 'end' statement */
            else
                D <= ~D; /* since D is only 1 bit, the
                        subtraction basically inverts the
                        value of D. */
        end
    end
endmodule


module And(input a, input b, output reg c);
    always @(a or b)
        c <= a & b; /* removed 'assign' assignment since 'c' is a
                    reg */
endmodule

```

QUESTION 2

Kyle Loyka

Time	Signal	Event
0	A	0 → 1
0	B	1 → 0
0	C	0 → 1
10	X	1 → 0
10	Z	1 → 0
30	Y	1 → 1
40	P	0 → 1
40	Y	1 → 0
60	Q	0 → 1
70	P	1 → 1
80	Q	1 → 1
80	P	1 → 0
90	Q	1 → 1

 

```

//Kyle Loyka
//ECEN 449 - 503
//Homework 1
//Question 3

`timescale 1ns/1ps

module q3(
    input A,
    input B,
    input C,
    input D,
    output f
);

    /* internal nets */
    wire e,u,g,h,j,k,m,n,p,q,r,s,t;

    // A*B
    nand n0(e,A,B);
    nand n1(u,e,e); // u = A*B

    // C*D*B
    nand n2(g,C,D);
    nand n3(h,g,B);
    nand n4(j,h,h); // j = C*D*B

    // ~C
    nand n5(k,C,C); // k = ~C

    // A*~C
    nand n6(m,A,k);
    nand n7(n,m,m); // n = A*~C



    // (AB) + (CDB)
    nand n8(p,u,u);
    nand n9(q,j,j);
    nand n10(r,q,p); // r = [AB + BCD]

    // [(AB) + (CDB)] + (A*~C)
    nand n11(s,n,n);
    nand n12(t,r,r);
    nand n13(f,s,t); // f = AB + CBD + A*~C

endmodule

```

QUESTION 4

  

C

	A	B
0	receive	send
1	send	receive

```

//Kyle Loyka
//ECEN 449 - 503
//Homework 1
//Question 4,b

`timescale 1ns/1ps

module communication_module(
    inout D, // allows D to read and write
    input C,
    input read_data_port,
    output write_data_port
);

    /* module to handle communications of ONE module */

    /* when C is high, take data from the write_data_port and send it
       through D */
    bufif1 write(D,write_data_port,C);

    /* when C is low, read data from D and output it to read_data_port
       */
    bufif0 read(read_data_port,D,C);

endmodule

```